

How to Leverage Input High-Z Technology to Reduce Solution Power and Size

Sanjay Rajasekhar, Principal Analog Design Engineer, and
Arvind Shankar, Staff Design Evaluation Engineer

Abstract

Multiplexed (muxed) successive approximation register analog-to-digital converter (SAR ADC) applications have size and power constraints, often dictated by the per-channel analog signal chain design choices. This article describes why muxed SAR ADCs equipped with analog input high-Z (high impedance) technology are key to obtaining a substantial reduction in solution size and power, without compromising performance and accuracy.

Introduction

Muxed SAR ADCs are commonly used in applications where there is a need to constantly monitor multiple critical variables in the system. In optical communications applications, laser biasing could be monitored via optical power measurement, while EEG/ECG signals from electrodes could be monitored in VSM applications. These muxed applications have some common requirements:

- ▶ There are many channels to monitor. Generally, the ADC sequences through all the channels.
- ▶ The channel voltages are generally uncorrelated with each other.
- ▶ Tight constraints exist on system-level footprint and power.

Some challenges arise because of these requirements. As the ADC finishes a conversion on one channel, the sampling capacitor within the ADC is charged to the voltage of the channel. If this voltage on the sampling capacitor is substantially different from the voltage of the channel next in sequence, then the signal chain must be designed to settle the sampling capacitor to the new voltage accurately, in the allowed acquisition time. Traditionally, the solution to this problem has been to use a wideband driver amplifier, coupled with an RC filter. A typical signal chain is shown in Figure 1.

 


Figure 1. A signal chain with a traditional muxed SAR ADC.

The sensor could output a voltage or a current, and the sensor interface circuit could be an instrumentation amplifier or a trans-impedance amplifier, respectively. The capacitor is normally an NPO/COG type, as other types can cause significant distortion. NPO capacitors have high linearity but low density. The NPO capacitor is also chosen to be much larger in value than the ADC internal sampling capacitor. It performs two critical functions:

- ▶ Reduction of the kickback from the ADC sampling capacitor
- ▶ Reduction of the wideband noise of the signal chain by filtering the noise beyond the required settling bandwidth

In the traditional signal chain, one is forced to use a driver amplifier and a large capacitor per channel. Each driver amplifier could consume anywhere between tenths of a mA to a few mA. Each capacitor, including clearances, could take up around 1 mm² of the board area. Replicating this signal chain over many channels has significant adverse effects on the system footprint and power consumption. This constitutes one of the major problems in muxed SAR ADC applications today.

 


Figure 2. Phases of the AD4696 with high-Z enabled and disabled.

What Is Input High-Z Technology?

The term high-Z technology, in the context of analog input, refers to a collection of circuit techniques that—without consuming static or continuous power—substantially increase the effective input impedance of the ADC. This makes the input of the ADC easy to drive.

Let's assume that the muxed ADC is converting on Channel N - 1 and that the next channel to be converted is Channel N.

At the rising edge of convert start (CNV), the channel voltage is sampled. In Figure 2, the first rising edge of CNV samples the voltage on Channel N - 1. The ADC then converts the sampled voltage on Channel N - 1. After the conversion, with the input high-Z disabled, the ADC proceeds to acquire the next channel in the sequence, which is Channel N. The voltage on Channel N can often be substantially different from the voltage on Channel N - 1, to which the ADC capacitor is now charged. This results in a huge voltage kick on Channel N (dark blue dashed line) and introduces a large error in the channel voltage at the sampling instant (second rising edge of CNV). This necessitates a large external capacitor to absorb the kick and a driver amplifier to supply the necessary charge.

When the input high-Z is enabled, the internal sampling capacitor of the ADC is charged up to the present voltage on the channel it is going to acquire before it begins the real acquisition. Immediately following the conversion on Channel N - 1,

a high-Z phase is introduced that accurately charges the ADC sampling capacitor to the present voltage on Channel N. This means that when the ADC sampling capacitor does connect to the external input, it doesn't source any charge and doesn't result in any kickback. In practice, there is usually a small residual error due to the charge injection of the internal switches (first charge kick). This small residual error results in practically negligible settling error at the sampling instant of Channel N. This charge error with the high-Z enabled would enable a massive improvement in the settling dynamics of the system.

When the sampling on Channel N is done, the ADC must proceed to do the conversion. So, the internal switches disconnect the ADC sampling capacitor from the external input. This results in a second charge kick due to the switch opening charge injection. Typically, the second charge kick has longer time to settle, so the magnitude of the first charge kick determines the settling error on a channel. Therefore, the first charge kick magnitude must be minimized.

The input high-Z technology is incorporated in the [AD4696](#) (latest generation muxed SAR ADC) as part of the EasyDrive™ feature set. As a result, the AD4696 begins acquisition on a channel extremely smoothly. It eliminates the need for a kickback absorption capacitor and a driver amplifier for each channel. This results in the massive reduction of the system footprint and power consumption, as well as a significant simplification of the signal chain, as shown in Figure 3.

 


Figure 3. A signal chain with the AD4696 muxed SAR ADC.

An important advantage of the input high-Z implemented in the AD4696 family is that the circuits that perform the high-Z function can all be power cycled at the rate of the conversion. So, the power consumption of the high-Z function would scale linearly with the throughput of the ADC, just like the core SAR ADC itself. This offers remarkable flexibility compared to the traditional, rather rigid signal chain designs.

The input high-Z function is also built into the [LTspice® model](#) of the AD4696. The first and second charge kicks are accurately modeled, enabling reliable simulation of the settling artefacts for signal chain designs.

Some Subtleties

Recall that the NPO capacitor also provided wideband noise filtering of the signal chain. Now that we want to eliminate the capacitor, we must find other ways to filter the noise. A simple way to achieve the same effective signal chain noise bandwidth is to increase the external series resistance. The AD4696 has a 60 pF internal capacitor in series with a 240 Ω typical internal resistor. By setting the external resistor, we can tune the signal chain noise bandwidth to a desired value.

Without the NPO capacitor, the external resistance plays an important role in the noise performance, linearity, and accuracy of the signal chain. A small value resistor can help settle sampling charge kicks quickly and thus improve linearity and accuracy, but it comes at the cost of increased overall noise due to higher effective noise bandwidth. Conversely, a large value resistor filters noise better, but it comes at the expense of degraded linearity and accuracy.

As described in the next section, a big advantage of the high-Z technology in AD4696 is that it allows large value resistors to be used (for better noise filtering) without degrading the linearity and accuracy. This allows optimization for all parameters in the signal chain—noise, linearity, accuracy, power, and solution size.

Measurement Results

Measurements have been performed with a 2 k Ω external resistor and without any NPO capacitor. The results show a massive improvement in AC and DC performance with the analog input high-Z enabled. The experiment involves running the core ADC of AD4696 at 1 MSPS but choosing an increasing number of channels as part of a round-robin sequence. Data are collected on one channel, while the other channels in the sequence are provided with 0 V inputs.

 


Figure 4. THD vs. number of channels in a sequence. Test tone: 1 kHz, -1 dBFS.

Figure 4 shows the distortion performance of the channel of interest for a 1 kHz, -1 dBFS tone. As the channels are sequenced with the high-Z disabled, nonlinear settling errors occur because the sampling capacitor is not charged to the subsequent channel voltage. This results in significant distortion. With the high-Z enabled, there is a massive improvement in the distortion performance.

 


Figure 5. DC settling errors in LSBs at 16-bit level.

Figure 5 shows the DC steady-state settling errors with and without the high-Z function. In this test, the channel of interest is provided with a near full-scale input and the other channels in the sequence are driven with 0 V. Conversions are performed on the channel of interest while adding an increasing number of channels to the sequence, and the shift in the average output code from the expected code is plotted.

When operating the core ADC at lower throughputs than 1 MSPS, the user may need to further lower the effective signal chain noise bandwidth to limit the analog front-end noise aliasing. This would necessitate higher resistance values, and the high-Z function helps immensely with maintaining the performance under these conditions.

Conclusion

The input high-Z technology implemented in the AD4696 family of parts offers unparalleled benefits for muxed SAR applications such as reduced system level power, reduced footprint, and reduced component count, to name a few, while maintaining high levels of AC performance and DC accuracy. It eliminates the need for a dedicated driver amplifier and a kickback absorption capacitor per channel. The power consumption for the high-Z function itself scales with the throughput of the ADC, offering remarkable flexibility and versatility for system-level design. An LTspice model of the AD4696 is available to simulate the effect of charge kicks in any system the user wishes to design.

Acknowledgement

The authors would like to thank Asif Ahmad, Peter Hurrell, and Tyler Schmitt for their contributions to this work.

About the Authors

Sanjay Rajasekhar is a principal analog design engineer in the Electronic Test and Measurement Group at Analog Devices. He joined ADI in 2008 and has a bachelor's degree in electronics and communications engineering from NITK-Surathkal, India. His areas of interest are high precision SAR and sigma-delta ADCs.

Arvind Shankar is a staff design evaluation engineer in the Process Control Converter Group at Analog Devices, Bangalore. He joined ADI in 2013 and has a bachelor's degree in electrical and electronics engineering and a master's degree in physics from BITS-Pilani, Goa, India.

Engage with the ADI technology experts in our online support community. Ask your tough design questions, browse FAQs, or join a conversation.



Visit ez.analog.com